
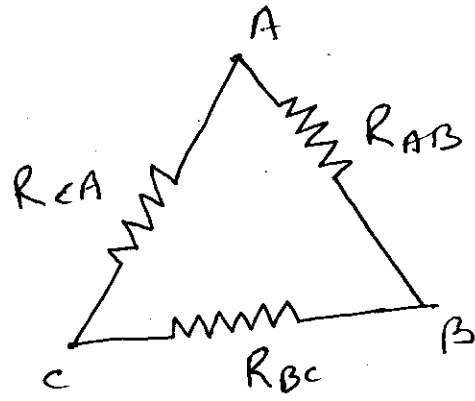


Ans. 3 (a)

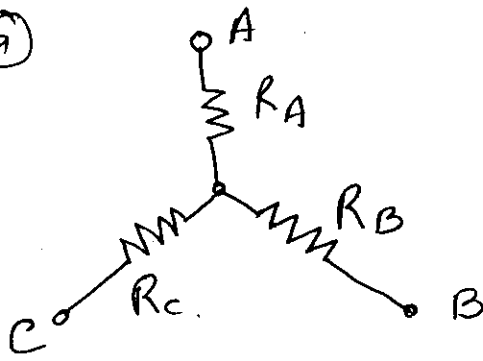

The two systems will be equivalent if the resistances measured between any pair of lines is same in both the systems.

→ Resistances between terminals A & B,

$$R_A + R_B = \frac{R_{AB}(R_{CA} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (i)}$$

→ Similarly, resistances b/w terminals B, C & C and A are

$$R_B + R_C = \frac{R_{BC}(R_{CA} + R_{AB})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (ii)}$$

and,

$$R_C + R_A = \frac{(R_{AB} + R_{BC})R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (iii)}$$

Add eqs. (i), (ii) and (iii), we get

$$R_A + R_B + R_C = \frac{R_{AB}R_{BC} + R_{BC}R_{CA} + R_{CA}R_{AB}}{R_{AB} + R_{BC} + R_{CA}}$$

On subtracting eqs. (ii), (iii) and (i) we get

$$R_A = \frac{R_{AB}R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (a)}$$

$$R_B = \frac{R_{AB} R_{BC}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (b)}$$

$$\text{and } R_C = \frac{R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (c)}$$

from eq. (a), (b) (c)

$$R_A R_B + R_B R_C + R_C R_A = \frac{R_{AB} R_{BC} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (d)}$$


Dividing eq. (d) by eq. (a), (b) and (c) respectively, we get

$$R_{AB} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_C}$$



$$R_{BC} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_A}$$

$$\text{and } R_{CA} = \frac{R_A R_B + R_B R_C + R_C R_A}{R_B}$$

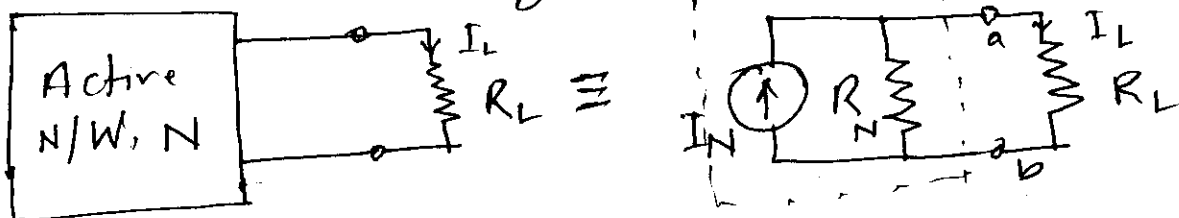Norton's Theorem: - A linear 2-terminal active network  $N$  consisting of independent and/or dependent voltage and current sources and resistors can be replaced at a pair of terminals  $a-b$  by equivalent network consisting of a single current source  $I_N$  in parallel with a single resistor  $R_N$ .



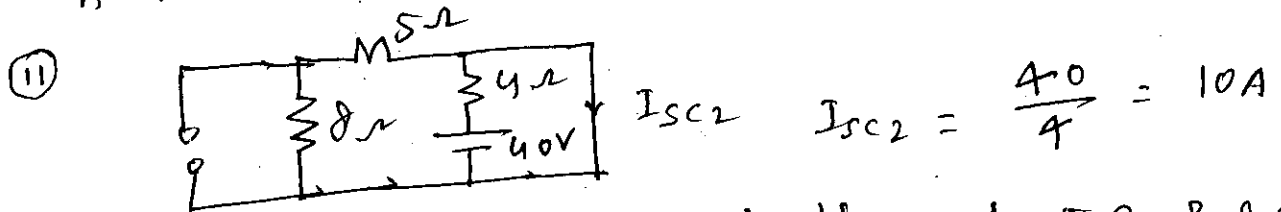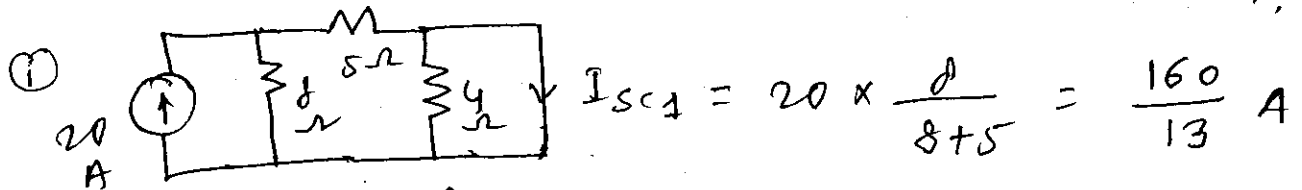
Ans 3 (b) Using superposition theorem, (11)




[ current through  $5\Omega$  &  $8\Omega$  resistors will be 0 ]

$$\therefore I_H = I_{sc1} + I_{sc2} = \frac{290}{13} \text{ A}$$

for  $R_N$ :

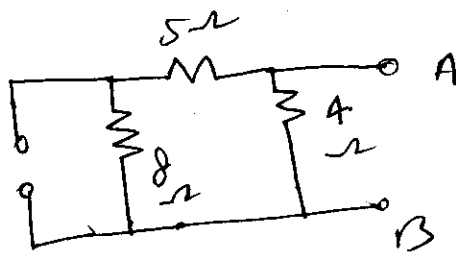
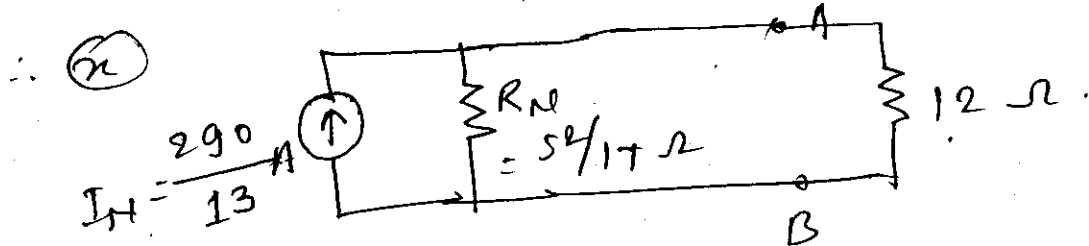
$$R_N = 4 \parallel 13 = \frac{52}{17} \Omega$$




(y) Max. power provided to R

$$= \frac{V_{Th}^2}{4R_L} \quad \text{as } V_{Th} = \frac{290}{13} \times \frac{52}{17}$$

and  $R_L = R = 12\Omega$

$$= 21.437 \text{ kW}$$

Ans 4 (a) series resonance

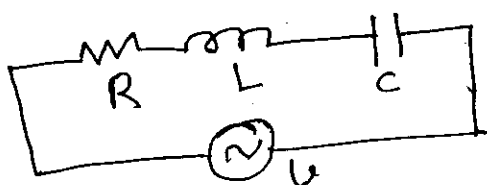

Impedance


$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

At freq.  $f_0$  of applied voltage  $U$ ,

$$X_L = X_C$$

$$\therefore 2\pi f_r L = \frac{1}{2\pi f_r C}$$

Phasor diagram

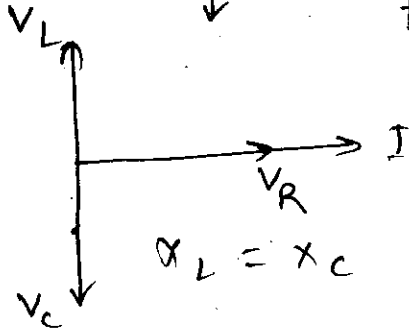

$$\therefore f_r = \frac{1}{2\pi \sqrt{LC}} \rightarrow \text{resonant freq.}$$

where  $V = IR$



$$V_C = IX_C \text{ \& } V_L = IX_C$$

if  $X_L > R$  or  $X_C > R$

$V_L > V$  or  $V_C > V$ , applied volt.

— called Voltage Resonance.

Parallel Resonance →

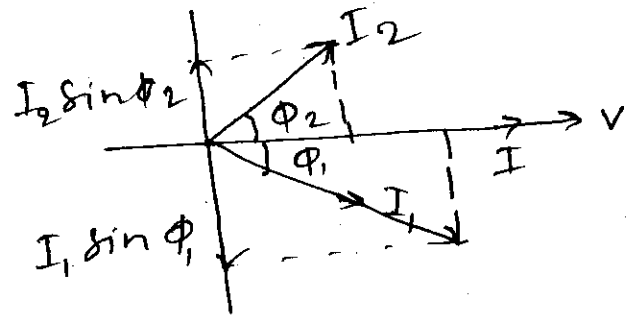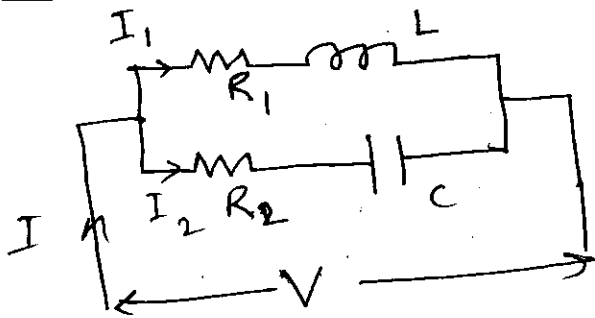

Ckt. will be in resonance when net Reactive component of current = 0.

$$\Rightarrow I_1 \sin \phi_1 = I_2 \sin \phi_2 \quad \text{--- (1)}$$

$$\text{as } I_1 = \frac{V}{\sqrt{R_1^2 + (\omega_r L)^2}}, \quad \sin \phi_1 = \frac{\omega_r L}{\sqrt{R_1^2 + (\omega_r L)^2}}$$

$$I_2 = \frac{V}{\sqrt{R_2^2 + \left(\frac{1}{\omega_r C}\right)^2}}, \quad \sin \phi_2 = \frac{1/\omega_r C}{\sqrt{R_2^2 + \left(\frac{1}{\omega_r C}\right)^2}}$$

Putting these value in eq (1), we get

$$\omega \quad f_r = \frac{1}{2\pi \sqrt{LC}} \sqrt{\frac{CR_1^2 - L}{CR_2^2 - L}} \quad \text{as } \omega_r = 2\pi f_r$$

if  $R_1 = R_2 = 0$ . then  $f_r = \frac{1}{2\pi\sqrt{LC}}$  (111)

Line current

$$I = I_1 \cos\phi_1 + I_2 \cos\phi_2$$


$$= \frac{V}{(L/RC)}$$

Similarities and dissimilarities: -

Under resonance condition: -

- |       | Series Resonance                  | Parallel Resonance   |
|-------|-----------------------------------|--|
| (i)   | $Z = R$ , minimum,                | $Z = L/CR$ , maximum.  |
| (ii)  | $I = V/R$ , max.                  | $I = \frac{V}{L/CR}$ , min.  |
| (iii) | p.f. = 1                          | p.f. = 1   |
| (iv)  | $f_r = \frac{1}{2\pi\sqrt{LC}}$   | $f_r = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{CR_1^2 - L}{CR_2^2 - L}}$ |
| (v)   | Magnification in voltage          | Magnif. in current   |
| (vi)  | Bandwidth = $\frac{R}{2\pi L}$ Hz | B.W. = $\frac{R}{2\pi L}$ Hz.  |

Ans 4 (b)

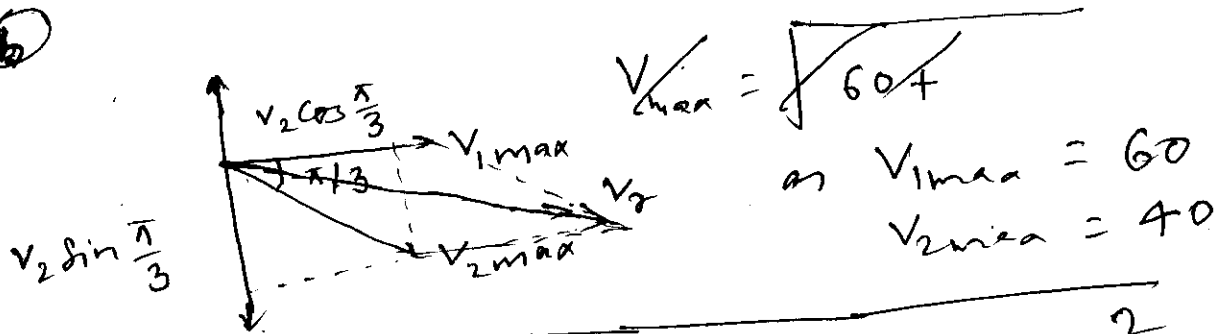


$$V_{max} = \sqrt{\left(V_{1m} + V_{2m} \cos \frac{\pi}{3}\right)^2 + \left(V_{2m} \sin \frac{\pi}{3}\right)^2}$$

$$= 87.178 \text{ V}$$

$$\phi = \tan^{-1} \left[ \frac{-V_{2m} \sin \frac{\pi}{3}}{V_{1m} + V_{2m} \cos \frac{\pi}{3}} \right] = -0.13 \pi \text{ radian}$$

$$\therefore V_r = 87.178 \sin(\omega t - 0.13\pi)$$

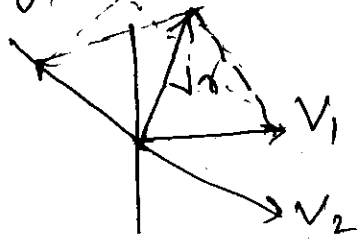Similarly, for diff.  $V_r = 52.915 \sin(\omega t + 0.227\pi)$



Ans 5 (a) Principle depends upon Magnetic, electrostatic, Electromagnetic induction, chemical and thermal effects.

Torques (i) Deflecting (ii) Controlling (iii) Damping.

(i) Deflecting torque  $\rightarrow T_d$

— In PMMC  $T_d = B i l N r$

$\Rightarrow T_d \propto i$

— In M.I,  $T_d = \frac{1}{2} I^2 \frac{dL}{d\theta}$

— In Dynamomt. Ins.  $T_d \propto i_f^2 \sin$

(ii) Controlling  $\begin{cases} \text{Spring Control} \\ \text{Gravity Control} \end{cases}$

(iii) Damping  $\begin{cases} \text{air friction} \\ \text{fluid friction} \\ \text{Eddy current} \end{cases}$

[Note: Explain every term in brief].

Ans 5 (b)

$$c = \frac{I_c}{2\pi f V} \quad \text{as } I_c = I \cos \phi_1 (\tan \phi_1 - \tan \phi_2)$$

(i)  $\text{as } \cos \phi_1 = 0.4$

$I = 0.75 \text{ A}$   $\text{as } \cos \phi_2 = 1$

$$\therefore C = 8.752 \mu F \quad \underline{\text{Ans.}}$$

(iv)

(ii) Similarly, for p.f. = 0.92 lagging

$$\cos \phi_1 = 0.4$$

$$\cos \phi_2 = 0.92$$

$$\therefore C = 7.125 \mu F \quad \underline{\text{Ans.}}$$

Ans 6 (a) MMF: magnetic potential that drives or tends to drive flux.  $\text{mmf} = NI \text{ (AT)}$

(b) Flux density: magnetic flux passing per unit area  $B = \frac{\Phi}{A}$ ;  $\text{Wb/m}^2$  or T.

Reluctance - property of material opposes the creation of magnetic flux.  $S = \frac{l}{\mu_0 \mu_r A}$   
unit AT/Wb.

Permeability: - Receptiveness of the material of having magnetic flux developed.

$$\mu = \frac{B}{H} \quad [\mu = \mu_0 \mu_r]$$

Magnetic ckt

Electric ckt.

(i) Driving force  $\rightarrow \text{MMF} = \Phi S$

$$\text{emf} = iR$$

(ii) Response  $\Phi = \frac{\text{mmf}}{S}$

$$i = \frac{\text{emf}}{R}$$

(iii)  $S = \frac{l}{\mu_0 \mu_r A}$

$$R = \rho \frac{l}{A}$$

(iv)  $B = \mu H$

$$J = \frac{E}{\rho}$$

(v)  $H = \frac{\text{mmf}}{l}$

$$E = \frac{V}{l}$$

(vi)

Ans 6 (b)

$$\eta = \frac{x V_2 I_2 \cos \phi}{x V_2 I_2 \cos \phi + P_i + x^2 P_c}$$

at full-load  $x = 1$ .

$$\therefore 0.98 = \frac{200 \times 0.8}{200 \times 0.8 + P_i + P_c}$$

$$\therefore P_i + P_c = 3.265 \text{ kW} \quad \text{--- (I)}$$


At max. eff.  $x^2 P_c = P_i \Rightarrow \left(\frac{3}{4}\right)^2 P_c = P_i$  --- (II)

from (I) & (II):  $P_i = 1.175 \text{ kW}$   
 $P_c = 2.09 \text{ kW}$

At half load,  
( $x = \frac{1}{2}$ )

$$\eta_{1/2} = \frac{\frac{1}{2} \times 200 \times 0.8}{\frac{1}{2} \times 200 \times 0.8 + P_i + \frac{1}{4} P_c}$$
$$= 97.92 \% \text{ Ans}$$

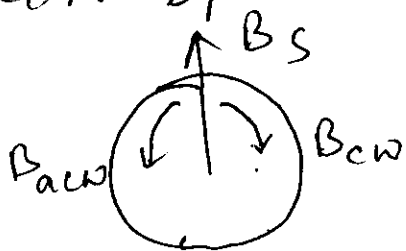Ans. 7 (a) Single phase induction motor has one phase on the stator winding. when supply is given, a pulsating magnetic field is produced. This pulsating magnetic field is not rotating. At zero speed net torque is ~~zero~~ zero.



$B_s \rightarrow$  Pulsating magnetic fd  
 $B_{cw} \rightarrow$  clockwise magnetic fd


$B_{acw} \rightarrow$  Anticlockwise mag. fd.

Continue... 7 (a)



(v)

Method of starting

(i) split phase motor

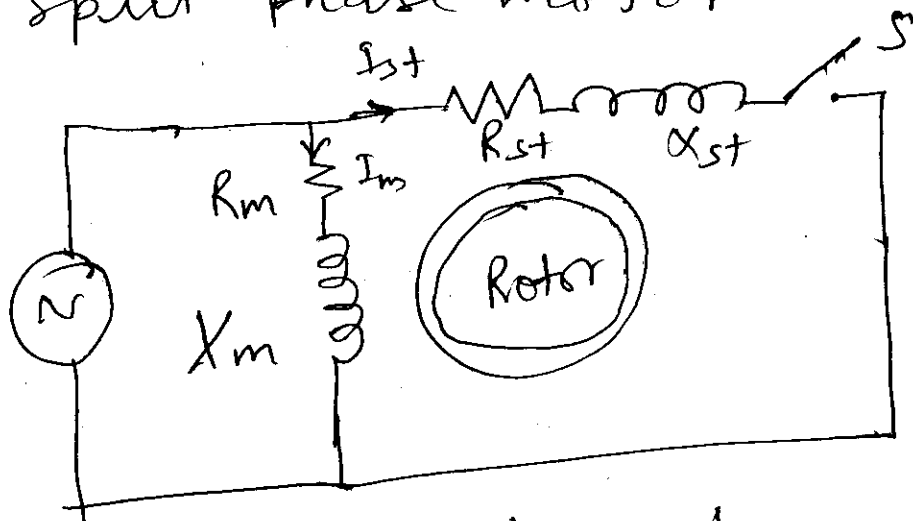

(ii) capacitor start motor

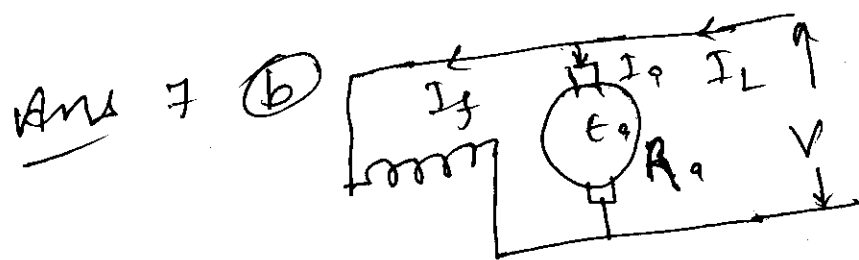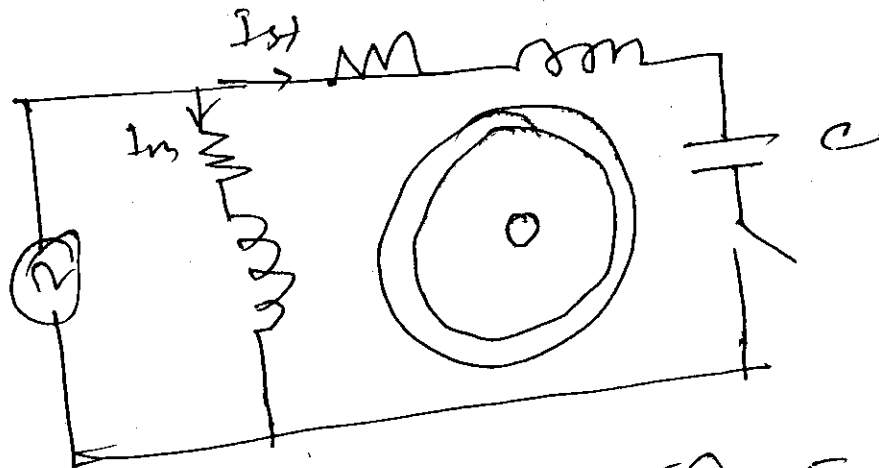

(c)  $E_{b0} = V - I_{a0} R_a$   
 $= 230 - 10 \times 0.1$   
 $= 229 \text{ V}$  Ans

$E_{bf} = V - I_{af} R_a = 230 - 100 \times 0.1$   
 $= 220 \text{ V}$  Ans

(d)  $\frac{T_f}{T_0} = \frac{E_{bf} I_{af}}{E_{b0} I_{a0}} \times \frac{N_0}{N_f}$   
 $= \frac{220 \times 100 \times 1500}{229 \times 10 \times 1470}$   
 $= 9.8$  Ans

$$\textcircled{7} \quad E_g = V + I_a R_a = 220 + 100 \times 0.1 \\ = 230 \text{ V}$$

$$\therefore N_g = N_f \frac{E_g}{E_{bf}} \times \frac{\Phi_m}{\Phi_f}$$

$$= 1470 \times \frac{230}{220} \times 1 =$$

$$= 1536.8 \text{ rpm.}$$