

UNIT-2

Q-1) When an PNP transistor is saturated its V_{ce}

- (a) Is zero and I_c is zero (b) is low and I_c is high.
 (c) Equal to V_{cc} and I_c is zero (d) Equal to V_{cc} and I_c is high


Q-2 If, in a bipolar junction transistor, $I_B = 100 \mu A$ and $I_C = 10 mA$ in what range does the value of its beta lie.

- ~~(a) V_{cc}~~ (a) 0.1 to 1.0 (b) 1.01 to 10
 (c) 10.1 to 100 (d) 100.1 to 1000

Q-3 The value of total collector current in a CB circuit is

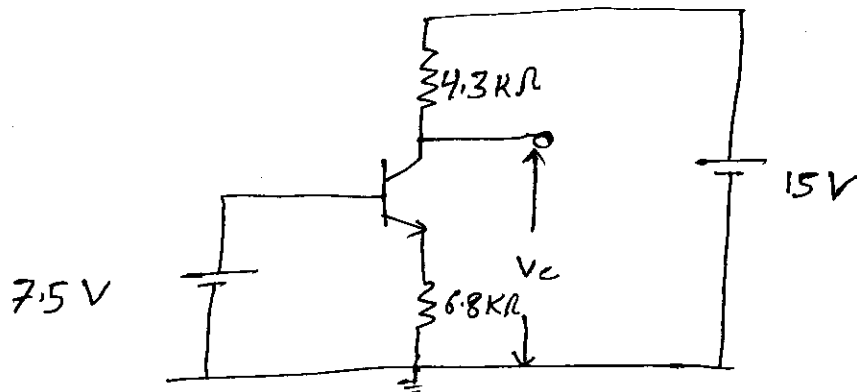
- (a) $I_c = \alpha I_E$ (b) $I_c = \alpha I_E + I_{c0}$
 (c) $I_c = \alpha I_E - I_{c0}$ (d) $I_c = \beta I_E$

Q-4 The nearest value of V_c in the circuit shown below will be (consider β high)



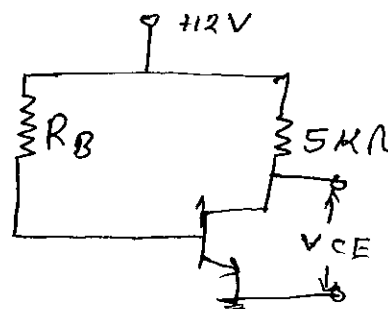- (a) 4V (b) 6.8V
 (c) 8.7V (d) 10.7V


Q-5 Consider $V_{BE} = 0.7V$ and $\beta = 50$ for the transistor in the circuit shown below, for $V_{CE} = 2V$, the value of R_B is



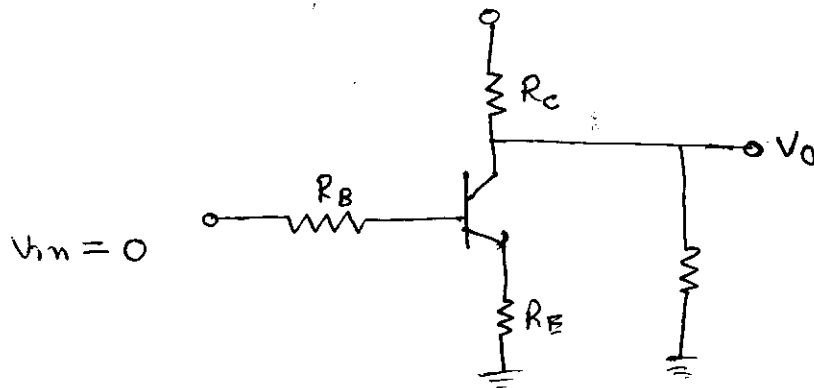- (a) 200kΩ (b) 242kΩ
 (c) 283kΩ (d) 300kΩ

Q-6

For the circuit shown below if $R_E = R_C = 1\text{ k}\Omega$, then the value of V_0 will be.



(a) 4.55V

(b) 2.5V

(c) 1V

(d) zero.

Q-7 The dc load line of a transistor circuit

(a) Has a negative slope (b) Is a curved line

(c) Gives graphic relation between I_C & I_B

(d) Does not contain the Q-point.

Q-8 \Rightarrow The positive swing of the output signal in a transistor circuit starts clipping first when Q-point of the circuit moves

(a) To the centre of the load line.

(b) Two-third way up the load line.

(c) Towards the saturation point.

(d) Towards the cut-off point.

Q-9. For a transistor amplifier with self-biasing network, the following components are used:

$R_1 = 4\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$ and $R_E = 1\text{ k}\Omega$ the approximate value of the stability factor 'S' will be

(a) 4

(b) 3

(c) 2

(d) 1.5

Q-10 - The emitter resistor R_E is bypassed by a capacitor C_E so as to improve the stability of Q point. (True/False)

Q-11 To obtain distortionless output, the Q-point in a voltage amplifier is selected in the middle of the active region (True/False)

Q-12 → when BJT is employed as an amplifier, it operates

- (a) In cut-off (b) In saturation
(c) into active region (d) reverse saturation

Q-13 - A FET is essentially a

- (a) current driven device (b) voltage driven device
(c) Power driven device (d) None of these

Q-14 - A JFET has three terminals, namely. ---

- (a) Cathode, anode, grid (b) emitter, base, collector
(c) source, gate, drain (d) none of these

Q-15 - A JFET is also called transistor.

- (a) unipolar (b) Bipolar
(c) Unijunction (d) None of these

Q-16 - A MOSFET can be operated with ---

- (a) Negative Gate Voltage only
(b) Positive Gate voltage only
(c) Positive as well as negative Gate voltage.
(d) None of these.

Q-17 A JFET has high input impedance because

- (a) It is made of semiconductor material
- (b) Input is reverse biased
- (c) of impurity atoms
- (d) None of the above.

Q-18 - which of the following devices has the highest input impedance?

- (a) JFET (b) MOSFET
- (c) Crystal diode (d) ordinary transistor

Q-19 - The drain current I_D in a JFET is given by

- (a) $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$ (b) $I_D = I_{DSS} \left(1 + \frac{V_{GS}}{V_P}\right)^2$
- (c) $I_D = I_{DSS} \left(1 - \frac{V_P}{V_{GS}}\right)^2$ (d) $I_D = I_{DSS} \left(1 + \frac{V_P}{V_{GS}}\right)^2$

Q-20 - For $V_{GS} = 0V$, the drain current becomes constant when V_{DS} exceeds - - -

- (a) cut off (b) V_{DD}
- (c) V_P (d) $0V$

Q-21 - An ideal op-amp has

- (a) infinite A_v (b) infinite R_i
- (c) zero R_o (d) All the above

Q-22 → The gain of actual op-amp is - approx

- (a) 1×10^6 (b) 1×10^4
- (c) 1×10^3 (d) 100

Q-23 - An inverting amplifier has $R_f = 2M$ and $R_i = 1k\Omega$, the closed loop gain is

- (a) -2000 (b) 2000
(c) -2001 (d) 2001

Q-24 - In binary numbers, shifting the binary point one place to the right.

- (a) Multiplies by 2 (b) Divides by 2
(c) Decrease by 10 (d) Increase by 10


Q-25 - the 2's complement of 1000_2 is

- (a) 0111 (b) 0101
(c) 1000 (d) 0001

Q-26 A XOR gate produces an output only when its two inputs are

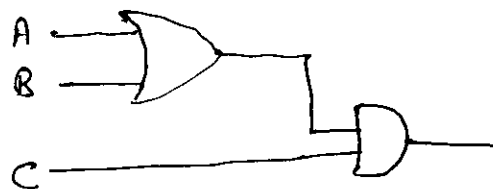
- (a) High (b) low
(c) different (d) same

Q-27 - To get an output 1 from circuit shown below the input ABC must be



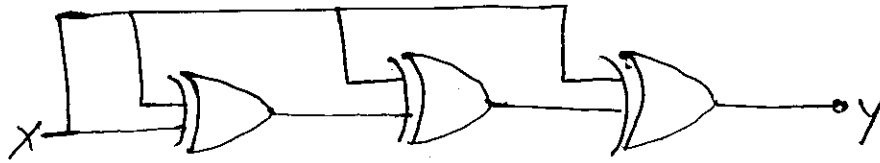- (a) 010 (b) 100
(c) 101 (d) 110

Q-28 - The output y of the circuit is given as



(a) 1

(b) Zero

(c) X

(d) \bar{X}

Q-29 - According to boolean algebra $(A+AB)$ equal to

(a) A

(b) B

(c) AB

(d) 1

Q-30 - A K-map of n -variables contains cells

(a) n

(b) $n+1$

(c) 2^n

(d) 2^{n-1}

Q-31 - The dual of the statement $(A+1)=1$ is

(a) $A \cdot 1 = A$

(b) $A \cdot 0 = 0$

(c) $A+A=A$

(d) $A \cdot A = 1$