

Q1(a) For mesh ADEFGA (using kirchoff's voltage law)

$$-(I_1 - I_2)1 + V_x - (I_1 - I_3)5 + 12 = 0$$

$$\text{or, } V_x + 12 = (I_1 - I_2) + (I_1 - I_3)5$$

$$V_x + 12 = 6I_1 - I_2 - 5I_3 \quad \text{--- (1)}$$

For mesh CHED

$$-4I_3 - 5(I_3 - I_1) - V_x - (I_3 - I_2)3 = 0$$

$$-V_x = 4I_3 + 5I_3 - 5I_1 + 3I_3 - 3I_2 = 0$$

$$\text{or } -V_x = 12I_3 - 5I_1 - 3I_2 = 0 \quad \text{--- (2)}$$

In mesh BCDA

$$-2I_2 - 3(I_2 - I_3) - (I_2 - I_1)1 = 0$$

$$-6I_2 + I_1 + 3I_3 = 0$$

$$\text{or } I_1 - 6I_2 + 3I_3 = 0 \quad \text{--- (3)}$$

Add (1) and (2)

$$12 = I_1 - 4I_2 + 7I_3 \quad \text{--- (4)}$$

The current relation between the source current and mesh current  $I_s = I_1 - I_3$   $\rightarrow$  (5)

Equation (3) is multiplied by (2) and (4) is multiplied by three and then add

$$2I_1 - 12I_2 + 6I_3 = 0$$

$$+ 36 = 3I_1 - 12I_2 + 21I_3$$

$$\hline -I_1 - 15I_3 = -36$$

$$\text{or } I_1 + 15I_3 = 36 \quad \text{--- (6)}$$

from (5)  $I_1 + 15I_3 = 36$

$$I_1 - I_3 = 4$$

AM

or,  $16 I_3 = 32$


$I_3 = 2 A$

$I_1 = 6 A$

Putting  $I_1$  and  $I_3$  in above eqn (4)

$I_2 = 2 A$

1. (b)

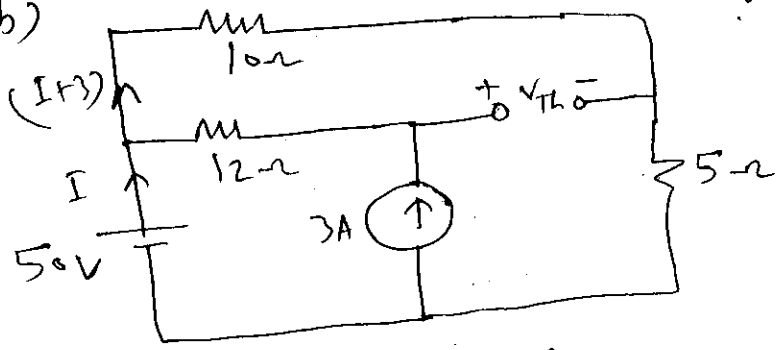

For finding  $V_{th}$  cut will be as

Using KVL in outer loop


$15(I+3) - 50 = 0$

$I = \frac{10}{3} - 3 = \frac{1}{3} A$

$10(I+3) - V_{th} + 12 \times 3 = 0$

$V_{th} = 36 + 10(I+3) = 36 + 10(\frac{1}{3} + 3)$   
 $= \frac{208}{3} V = V_{th}$


for  $R_{th}$

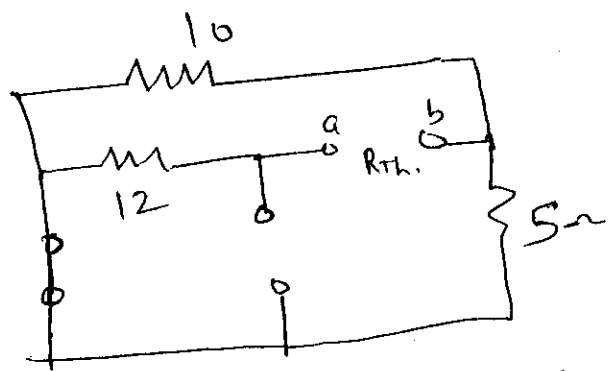


$R_{th} = (\frac{10 \times 5}{10+5}) + 12 = \frac{46}{3}$

$I_L = \frac{208/3}{\frac{46}{3} + 2} = 4 A$

Q 2 (a)

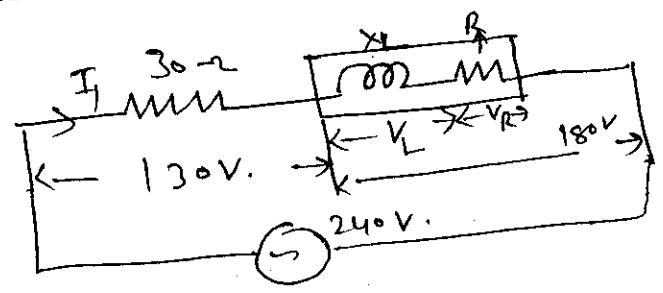

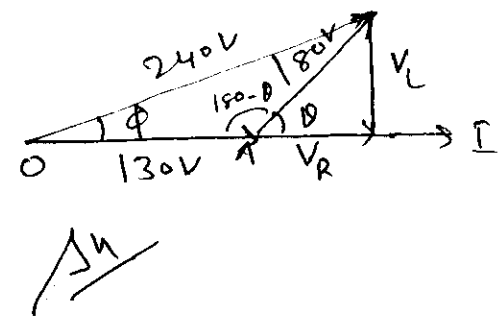Power absorbed by Coil  
 $P = 180 I \cos \phi$



Q2 Contd:

$$= 180 \times 4.33 \times \cos \theta$$

Cos  $\theta$  from laws of  $\Delta$ 

$$\cos(180 - \theta) = \frac{130^2 + 180^2 - 240^2}{2 \times 130 \times 180}$$

$$\cos \theta = \frac{130^2 + 180^2 - 240^2}{2 \times 130 \times 180}$$

$$\cos \theta = \frac{240^2 - 130^2 - 180^2}{2 \times 130 \times 180} = 0.177 \text{ lags}$$

$$V_L = 180 \sin \theta = 180 \sqrt{1 - \cos^2 \theta} = 177.16$$

$$X_L = V_L / I = \frac{177.16}{4.33} = 40.9 \Omega$$

$$L = \frac{X_L}{2\pi f} = \frac{40.9}{2\pi \times 50} = 0.13 \text{ H.}$$

$$V_R = 180 \cos \theta = 180 \times 0.177 = 31.86 \text{ V}$$

$$R = V_R / I = \frac{31.86}{4.33} = 7.36 \Omega$$

$$\text{Pf } \cos \phi = \frac{130 + V_R}{240} = \frac{130 + 31.86}{240} = 0.674$$

Q2(b) For half cycle

$$V_{av} = \frac{\text{Area of half cycle}}{\text{Base length of half cycle}}$$

$$= \frac{(\frac{1}{2} \times 2 \times 4) + \frac{1}{2} \times 2 \times 4}{4} = 2 \text{ V.}$$

Another Method.

$$V_{av} = \frac{1}{4} \left[ \int_0^2 v_1(t) dt + \int_2^4 v_2(t) dt \right]$$

$$v_1(t) = mt + c \Rightarrow 2t + 0 = 2t$$

$$v_2(t) = -2t + c \text{ for } t = 4, v_2 = 0, c = 8$$

$$v_2(t) = (-2t + 8)$$

~~V<sub>rms</sub> =~~

SM

$$V_{r.m.s} = \sqrt{\frac{1}{4} \left[ \int_0^2 v_1^2(t) dt + \int_2^4 v_2^2(t) dt \right]}$$

$$= 2.30 V.$$

gk A

Q3 (a)  $Z_{ph} = \sqrt{10^2 + 10^2}$   
 $= 10\sqrt{2}$

$V_{ph} = 400/\sqrt{3} = 231 V$

$I_L = I_{ph} = 231/10\sqrt{2} = 16.33 A$

$\phi = \tan^{-1} X_{ph}/R_{ph} = \tan^{-1} \frac{10}{10} = 45^\circ$

$P.f. = (\cos \phi) = \cos 45 = .707$

Total power =  $\sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 16.33 \times .707$   
 $= 8000 W$

$W_2 + W_1 = 8000$  — (1)

$\tan \phi = \sqrt{3} \frac{W_2 - W_1}{W_2 + W_1}$  or  $W_2 - W_1 = 4619 \text{ watt}$  — (2)

gk A from (1) and (2)  $W_2$  and  $W_1$  can be obtained.

$Z_{ph} = 10\sqrt{2}$

$V_{ph} = V_L/Z_{ph} = \frac{400}{10\sqrt{2}} = 28.28 A$

$I_L = \sqrt{3} I_{ph} = \sqrt{3} \times 28.28 = 48.98 A$

$\cos \phi = \cos 45^\circ = 1/\sqrt{2}$

Total power =  $\sqrt{3} V_L I_L \cos \phi = 23995 W$

$W_2 + W_1 = 23995$  — (1)

$\tan 45^\circ = \sqrt{3} \frac{W_2 - W_1}{W_2 + W_1}$  or  $W_2 - W_1 = 13854$  — (2)

from (1) and (2)  $W_1$  and  $W_2$  can be obtained

3 (b) Energy consumed in 11 hrs =  $\frac{150}{1000} \times 11 = 1.65 \text{ kWh}$ .

Revolution made by disc in 11 hr. = Speed of disc in rpm  $\times$  time in min  
 $= 3.5 \times 11 \times 60 = 2310$

Energy Consumption recorded by meter =  $\frac{\text{Revolution made by disc}}{\text{meter constant}}$   
 $= \frac{2310}{1300} = 1.777 \text{ kWh}$

AM

Recording error =  $1.777 - 1.65$   
 =  $0.127$  (Excess)

% error =  $\frac{1.777 - 1.65}{1.65} \times 100$

Q 4(a)  $I_0 = 3A$ ,  $\cos \phi_0 = 0.25$   $\phi_m = ?$   
 $V_1 = 230V$ ,  $f = 50Hz$   $W_0 =$  input power at no load = Core loss  
 $N_1 = 300$

$E_1 = 4.44 f \phi_m N_1$   
 $230 = 4.44 f \phi_m N_1$

i)  $\phi_m = \frac{230}{4.44 \times 50 \times 300}$   
 =  $3.453$  mwb.

[ $\because E_1 = 4.44 \phi_m f N_1$ ]

ii) input power at no load = Core loss  
 $W_0 = V_1 I_0 \cos \phi_0 = 230 \times 3 \times 0.25 = 172.5$  watt.

iii)  $I_m = I_0 \sin \phi_0 = 3 \sqrt{1 - \cos^2 \phi_0}$   
 =  $3 \sqrt{1 - (0.25)^2} = 2.905A$ .

Q 4 (b) Given  $kVA = 100$ ,  $\frac{V_1}{V_2} = \frac{6600V}{400V}$   $P_i = 600$  watt  
 $P_c (fl) = 900$  watt  
 P.f. =  $0.8$  lag

i)  $\eta$  at full load

%  $\eta_{fl} = \frac{kVA \times \cos \phi \times 1000}{kVA \times \cos \phi \times 1000 + P_i + P_c(fl)} \times 100$   
 =  $\frac{100 \times 0.8 \times 1000}{100 \times 0.8 \times 1000 + 600 + 900} \times 100 = 98.15\%$


ii)  $\eta$  at half load:

cu loss at  $\frac{1}{2}$  load =  $(\frac{1}{2})^2 \times 900 = 225$  watt  
 $kVA$  at  $\frac{1}{2}$  load =  $\frac{1}{2} \times 100 = 50$  kVA.

%  $\eta$  at half load =  $\frac{50 \times 0.8 \times 1000}{50 \times 0.8 \times 1000 + 600 + 225} \times 100 = 97.98\%$   
 load correspond to max  $\eta = kVA \times \sqrt{\frac{P_i}{P_c(fl)}} = 100 \times \sqrt{\frac{600}{900}} = 81.64$  kVA

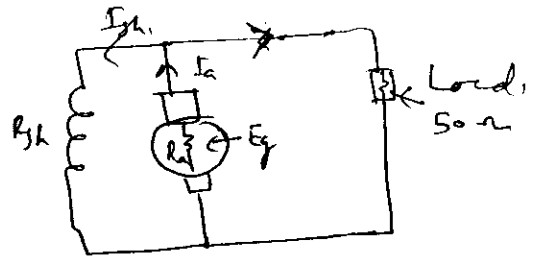(6)

5(a)  $R_a = 1 \Omega$       $R_L = 50 \Omega$   
 $R_{sh} = 2000 \Omega$   
 $\Phi = 25 \times 10^{-3} \text{ wb}$ ,  $N = 1000 \text{ r.p.m}$



$Z =$  No of conductors in armature wdg.  
 $=$  no of slots  $\times$  No of conductor per slot  
 $= 40 \times 12 = 480$

$$E_g = V_t + I_a R_a \quad \text{--- (1)}$$

$$E_g = \frac{\Phi P Z N}{60 A} = \frac{4 \times 25 \times 10^{-3} \times 1000 \times 480}{60 \times 2} = 400 \text{ V}$$

To calculate  $I_a$  [ Total resistance to be findant)

$$R_T = R_a + (R_{sh} \parallel R_L) = 41 \Omega$$

$$I_a = E_g / R_T = \frac{400}{41} = 9.76 \text{ A}$$

Putting  $I_a$  in (1)

$$E_g = V_t + 9.76 \times 1$$

$$V_t = 400 - 9.76 = 390.24 \text{ volts}$$

for lap wound  $A = P = 4$



$$E = \frac{\Phi P Z N}{60 A} = \frac{4 \times 25 \times 10^{-3} \times 1000 \times 480}{60 \times 4} = 200 \text{ V}$$

$$I_a = \frac{200}{41} = 4.88$$

$$V_t = 200 - 4.88 = 195.12$$

SH

5 (4)

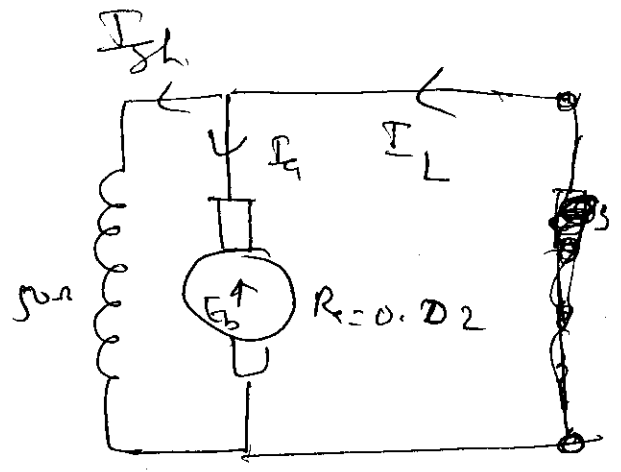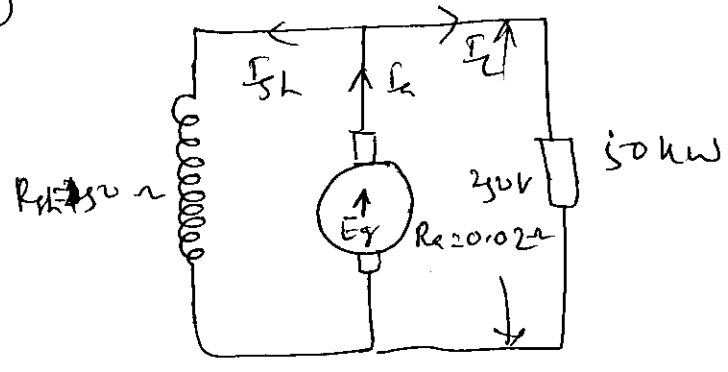

$N_g = 400 \text{ r.p.m}$

Load = 50kw,  $R_g = 0.02$ ,  $R_{sh} = 50$ ,  $I_L = \frac{50 \times 1000}{250} = 200 \text{ A}$

$V = 250 \text{ V}$

as gen

$I_a = I_L + I_{sh}$

$I_a = 205 \text{ A}$

$E_g = V + I_a R_g = 250 + 0.02 \times 205$

As motor

$I_a = I_L - I_{sh}$

$I_a = 195 \text{ Amp}$

$E_b = V - I_a R_g = 250 - 0.02 \times 195$

Now for shunt M/c  $N_g \propto E_g$  and  $N_b \propto E_b$

$\frac{E_g}{E_b} = \frac{N_g}{N_b}$

or,  $\frac{250 + 0.02 \times 205}{250 - 0.02 \times 195} = \frac{400}{N_b}$  or,  $\frac{254.1}{246.1} = \frac{400}{N_b}$

or,  $N_b = 387.40 \text{ r.p.m}$

(6)

i)  $N_s = \frac{120f}{p} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m}$

ii)  $s = \frac{N_s - N}{N_s}$

or  $s N_s = N_s - N$

or,  $N = N_s (1 - s) = 1500 (1 - 0.04) = 1440 \text{ r.p.m}$

iii)

$s' = \frac{N_s - N}{N_s} = \frac{1500 - 1440}{1500} = 0.6$

$f' = s' f = 0.6 \times 50 = 30 \text{ Hz}$

Signature